

1. 什么是EDA?

答: Electronic design automation, 一般翻译为中文「电子设计自动化」 EDA技术就是以微电子技术为先导, 现代电子技术为灵魂, 计算机软件技术为手段, 最终形成集成电子系统或专用集成电路为目的的一种新兴技术。EDA技术就是依靠功能强大的电子计算机, 在EDA工具软件平台上, 对以硬件描述语言为系统逻辑描述手段完成的设计文件, 自动地完成逻辑编译、化简、分割、综合、优化和仿真, 直至下载到可编程逻辑器件CPLD/FPGA或专用集成电路ASIC芯片中, 实现既定的电子电路设计功能。

极大地提高了设计效率, 缩短了设计周期, 节省了设计成本。

2. 什么是FPGA?

答: FPGA (Filed Programmable Gate Array) : 现场可编程逻辑门阵列。FPGA器件及其开发系统是开发大规模数字集成电路的新技术。它利用计算机辅助设计, 绘制出实现用户逻辑的原理图、编辑布尔方程或用硬件描述语言等方式作为设计输入; 然后经一系列转换程序、自动布局布线、模拟仿真的过程; 最后生成配置FPGA器件的数据文件, 对FPGA器件初始化。

3. Quartus**的开发流程? **

答: ①建立一个工程文件;

工程文件名应与实体名保持一致, 以字母开头, 不以下划线结尾。

②建立一个VHDL文件, 输入程序文本并保存;

注意设计相应的VHDL文件为顶层实体。

③对VHDL程序进行编译, 并在当前文件夹创建模型文件;

④建立一个原理图文件, 插入刚刚建立的模型文件并保存;

注意保存名字不与实体名一样, 否则会报错;

⑤设计该原理图文件为顶层实体, 并进行编译;

⑥按照所给的说明书分配引脚;

⑦建立一个波形文件并保存, 植入节点名, 设计好波形进行仿真验证;

需先设置为功能性仿真, 并产生一个功能仿真网络表, 再运行仿真。

⑧若仿真验证通过, 则再一次进行重新编译;

⑨若编译正确则会形成以sof、pof为后缀的下载文件;

⑩用JTAG口下载到FPGA进行结果验证。

4. VHDL**的构成? **

答: 一个VHDL设计由若干个VHDL文件构成, 每个文件主要包含如下三个部分中的一个或全部: 程序包、实体、结构体。

一个相对完整的VHDL程序, 通常由库、程序包、实体、结构体、配置组成。语言特点是有并行语句和顺序语句组成。

(1) 动态扫描VHDL描述语言（包含分频器、60倒计时计数器、动态扫描）：

```
library ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

entity dtsm_all is

port(clk_50M:in std_logic;

      seg,dig:out std_logic_vector(7 downto 0);

      rb,en,load:in std_logic;

      a:in std_logic_vector(7 downto 0));

end dtsm_all;

architecture one of dtsm_all is

    signal daout:std_logic_vector(3 downto 0);

    signal q:std_logic_vector(7 downto 0);

    signal qg,qs:std_logic_vector(3 downto 0);

    signal clk_1,clk_1k,tclk_1,tclk_2:std_logic;

    signal cnt1:integer range 0 to 24999;

    signal cnt2:integer range 0 to 499;

    signal cnt8:std_logic_vector(2 downto 0);

begin

    qg<=q(3 downto 0);

    qs<=q(7 downto 4);

    clk_1k<=tclk_1;

    clk_1<=tclk_2;

    P1:process(clk_50M)  --分频 50M

    begin

        if(clk_50M'event and clk_50M='1') then

            if(cnt1=24999) then
```

```

• cnt1<=0;

• tclk_1<=not tclk_1;

else

• cnt1<=cnt1+1;

end if;

end if;

end process P1;

P2:process(clk_1k)  -- 分频1k

begin

if(clk_1k'event and clk_1k='1') then

if(cnt2=499) then

• cnt2<=0;

• tclk_2<=not tclk_2;

else

• cnt2<=cnt2+1;

end if;

end if;

end process P2;

P3:process(rb,clk_1,en,load,a)

begin

if(rb='0') then q<="00000000";

elsif(clk_1'event and clk_1='1') then

if(load='1') then q<=a;

elsif(en='1') then q<=q-1;

if(q<="00000000") then q<="00111011";

end if;

end if;

```

```

end if;

end process P3;

P4:process(cnt8,qg,qs)

begin

    case cnt8 is

        when "000"=>dig<="11111110";daout<=qg;

        when "001"=>dig<="11111101";daout<=qs;

        when "010"=>dig<="11111011";daout<=qg;

        when "011"=>dig<="11110111";daout<=qs;

        when "100"=>dig<="11101111";daout<=qg;

        when "101"=>dig<="11011111";daout<=qs;

        when "110"=>dig<="10111111";daout<=qg;

        when "111"=>dig<="01111111";daout<=qs;

        when others=>null;

    end case;

end process P4;

P5:process(clk_1k)

begin

    if(clk_1k'event and clk_1k='1') then

        cnt8<=cnt8+1;

    end if;

end process P5;

P6:process(daout)

begin

    case daout is

        when "0000"=>seg<="11000000";

        when "0001"=>seg<="11111001";

        when "0010"=>seg<="10100100";

```

```

when "0011" => seg <= "10110000";

when "0100" => seg <= "10011001";

when "0101" => seg <= "10010010";

when "0110" => seg <= "10000010";

when "0111" => seg <= "11111000";

when "1000" => seg <= "10000000";

when "1001" => seg <= "10010000";

when "1100" => seg <= "10001000";

when "1101" => seg <= "10000011";

when "1110" => seg <= "10000110";

when "1111" => seg <= "11000001";

when others => null;

end case;


end process P6;

end one;

```

编码器译码器

(2) 3-8线译码器:

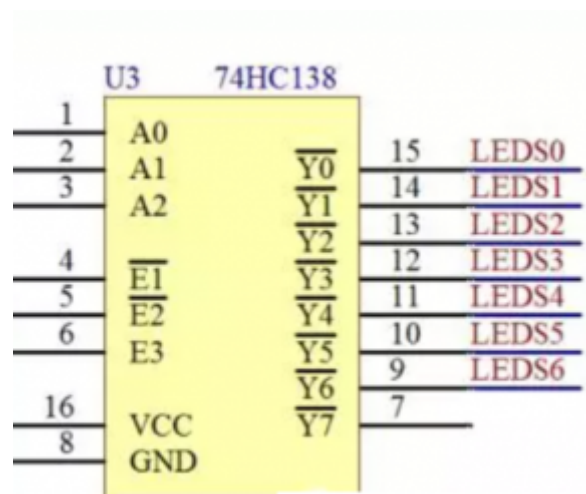

注意需要使能 E1 E2 低电平 E3高电平

```

library ieee;
use ieee.std_logic_1164.all;

```

```

entity decoder38 is
    port(
        en1,en2,en3,a1,a2,a3 : in std_logic;
        output : out std_logic_vector(7 downto 0)
    );
end entity;

architecture arch1 of decoder38 is
    signal address std_logic_vector(2 downto 0);
    begin process(en1,en2,en3,a1,a2,a3)
        if(en1 = '0 && en2 = '0' & en3 = '0')
            address <= a1&a2&a3;
            case address
                when "000" => output <= "11111110";
                when "001" => output <= "11111101";
                when "010" => output <= "11111011";
                when "011" => output <= "11110111";
                when "100" => output <= "11101111";
                when "101" => output <= "11011111";
                when "110" => output <= "10111111";
                when "111" => output <= "01111111";
            when
            else
                output <= "11111111";
            end if
        end process;
    end arch1;

```

(3) 8-3线编码器

```

library ieee;
use ieee.std_logic_1164.all;

entity encoder83 is
    port(
        input: in std_logic_vector( 7 downto 0);
        output : out std_logic_vector(2 downto 0);
    );
end encoder83;

architecture arch1 of encoder83 is
    begin
        process(input)
        begin
            case input
                when "11111111" then output<="000";
                when "11111110" then output<="001";
                when "11111101" then output<="010";
                when "11111011" then output<="011";
                when "11110111" then output<="100";
                when "11101111" then output<="101";
                when "11011111" then output<="110";
                when "10111111" then output<="111";
            end case;
        end process;
    end arch1;

```

```
        when others then null;
    end case;
end process
end arch1;
```

(4) 8-3线优先编码器

```
-- Code your design here
library IEEE;
use IEEE.std_logic_1164.all;

entity encoder83 is
    port(
        input : in std_logic_vector(7 downto 0);
        en1,en2,en3 : in std_logic;
        output : out std_logic_vector(2 downto 0)
    );
end encoder83;

architecture arch1 of encoder83
    p1: process(en1,en2,en3,input)
    begin
        if(en1 = '1' and en2 = '1' and en3 = '0')
            if(input(0) = '1') then
                output <= "000";
            end if;
            if(input(1) = '1') then
                output <= "001";
            end if;
            if(input(2) = '1') then
                output <= "010";
            end if;
            if(input(3) = '1') then
                output <= "011";
            end if;
            if(input(4) = '1') then
                output <= "100";
            end if;
            if(input(5) = '1') then
                output <= "101";
            end if;
            if(input(6) = '1') then
                output <= "110";
            end if;
            if(input(7) = '1') then
                output <= "111";
            end if;
        else
```

```

        output <= "xxx"
    end if;
end p1;
end arch1;

```

半加器 & 全加器 & 乘法器

(5) 半加器

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;

entity half_add is
    port(
        a,b : in std_logic;
        c,s : out std_logic;
    );
end half_add;

architecture arch1 of half_add is
    begin
        p1: process(a,b)
        begin
            c <= a xor b;
            s <= a and b;
        end process p1;
    end arch1;

```

(6) 全加器

```

library ieee;
use ieee.std_logic_1164.all;

entity full_adder is
    port(
        a,b,cin in std_logic;
        s,c out std_logic
    );
end full_adder;

architecture arch1 in full_adder is
    signal x std_logic_vector(2 downto 0);
    begin process(a,b,cin)
        x <= a&b&cin;
        case x is
            when "000"=>s<='0';cout<='0';

            when "100"=>s<='1';cout<='0';

```



```

        when "010" => s <= '1'; cout <= '0';

        when "110" => s <= '0'; cout <= '1';

        when "001" => s <= '1'; cout <= '0';

        when "101" => s <= '0'; cout <= '1';

        when "011" => s <= '0'; cout <= '1';

        when "111" => s <= '1'; cout <= '1';
    end case;
end process;
end arch1;

```

(7) 乘法器

```

library ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

entity mul is

port(x1,x2:in std_logic_vector(2 downto 0);

     y:out std_logic_vector(5 downto 0));

end mul;

architecture one of mul is

begin

y<=x1*x2;

end one;

```

触发器

(8) JK触发器

```

library ieee;
use iee.std_logic_1164.all;
entity JK_FF is
    port(
        J,K,CLK:in std_logic;
        Q,notQ:buffer std_logic
    );
end JK_FF;

```



```

architecture arch1 of JK_FF is
    signal P,notP : std_logic;
begin
    process(J,K,CLK)
    begin
        P <= Q;
        notP <= notQ;
        if( CLK event AND CLK = '1') then
            if(J = '0' AND K = '0') then
                P <= Q;
                notP <= notQ;
            elsif (J = '1' AND K = '0') then
                P <= '1';
                notP <= '0';
            elsif (J = '0' AND K = '1') then
                P <= '0';
                notP <= '1';
            else
                P <= not Q;
                notP <= not notQ;
            end if;
            Q <= P;
            notQ <= notP;
        end process;
    end arch1;

```

D触发器:

$$Q_{n+1} = D$$

  

```

library ieee;
use ieee.std_logic_1164.all;

entity D_FF is
    port(
        clk,D : in std_logic;
        Q,notQ : out std_logic
    );
end D_FF;

architecture arch1 of D_FF is
    process(clk,D)
    begin
        if (clk 'event and clk = '1')
            Q <= D;
            notQ <= not D;
        end if;
    end process
end arch1;

```

异步复位的D触发器:

```

library ieee;
use ieee.std_logic_1164.all;

entity D_FF is
    port(
        clk,D,reset : in std_logic;
        Q,notQ : out std_logic
    );
end D_FF;


architecture arch1 of D_FF is
    process(clk,D,reset)
    begin
        if(reset = '1') then --多了一个复位判断
            Q <= '0';
            notQ <= '1';
        else
            if (clk 'event and clk = '1') then
                Q <= D;
                notQ <= not D;
            end if;
        end if;
    end process
end arch1;

```

带使能端的8位可（不）移位寄存器

Order Number	Package Number	Package Description
DM74164	N14A	14-Lead Plastic Dual-In-Line Package (PDIP), JEDEC MS-001, 0.300 Wide

Connection Diagram

 

Function Table

Inputs				Outputs			
Clear	Clock	A	B	Q _A	Q _B	...	Q _H
L	X	X	X	L	L	...	L
H	L	X	X	Q _{A0}	Q _{B0}	...	Q _{H0}
H	↑	H	H	H	Q _{An}	...	Q _{Gn}
H	↑	L	X	L	Q _{An}	...	Q _{Gn}
H	↑	X	L	L	Q _{An}	...	Q _{Gn}

H = HIGH Level (steady state)
L = LOW Level (steady state)
X = Don't Care (any input, including transitions)
↑ = Transition from LOW-to-HIGH level
Q_{A0}, Q_{B0}, Q_{H0} = The level of Q_A, Q_B, or Q_H, respectively, before the indicated steady-state input conditions were established.
Q_{An}, Q_{Gn} = The level of Q_A or Q_G before the most recent ↑ transition of the clock; indicates a one-bit shift.

```
library ieee;
use ieee.std_logic_1164.all;

entity shiftReg is
    port(
        clk,en,load : in std_logic;
        D : in std_logic(7 downto 0);
        S : buffer std_logic(7 downto 0)
    );
end shiftReg;

architecture arch1 of shiftReg
    signal tmp : std_logic;
begin
    process(D,S,clk,en,load)
    begin
        if(en = '1') then
            if (clk' event AND clk = '1') then
                if(load = '1')
                    S <= D;
                    tmp <= 0;
                elsif (load = '0')
                    tmp <= D(0);
                    S(6 downto 0) <= D(7 downto 1)
                    S(7) <= tmp;
                end if;
            end if;
        end if;

        if(en = '0') then
            if(clk = '1') then
```

```

        S <= D;
    end if;
end if;
end process;
end arch1;

```

(10) 8选1数据选择器

```

library ieee;
use ieee.std_logic_1164.all

entity mux81 is
    port(
        a,b,c : in std_logic;
        inputData : in std_logic_vector(7 downto 0);
        outputData : out std_logic
    );
end mux81;

architecture arch1 of mux81 is
    signal address : std_logic_vector(2 downto 0)
begin
    begin process(a,b,c,inputData)
        address <= a&b&c; //并列操作 只对vector有效
        case address is
            when "000" => outputData <= inputData(0);
            when "001" => outputData <= inputData(1);
            when "010" => outputData <= inputData(2);
            when "011" => outputData <= inputData(3);
            when "100" => outputData <= inputData(4);
            when "101" => outputData <= inputData(5);
            when "110" => outputData <= inputData(6);
            when "111" => outputData <= inputData(7);
            when others => null;
        end case;
    end process;
end arch1;

```

(11)60进制加计数器

```

library ieee;

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

entity jsq60 is

    port(clk,reset:in std_logic;

```

```

    dout:out std_logic_vector(7 downto 0));

end jsq60;

architecture one of jsq60 is

    signal sge:std_logic_vector(3 downto 0);

    signal sshi:std_logic_vector(3 downto 0);

    begin

        dout(7 downto 4)<=sshi;

        dout(3 downto 0)<=sge;

        process(clk,reset)

        begin

            if(reset='0') then

                sge<="0000";

                sshi<="0000";

            elsif(clk'event and clk='1') then

                if(sshi<5) then

                    if(sge=9) then

                        • sge<="0000";

                        • sshi<=sshi+1;

                    else

                        • sge<=sge+1;

                    end if;

                else

                    if(sge=9) then

                        • sge<="0000";

                        • sshi<="0000";

                    else

                        • sge<=sge+1;


```

```

    •   end if;

    end if;

    end if;

end process;

end one;

```

与非门:

```

-- Code your design here
library IEEE;
use IEEE.std_logic_1164.all;

entity nand_gate is
    port(
        input_1,input_2 : in std_logic;
        output : out std_logic);
end nand_gate;

architecture arch1 of nand_gate is
    p1 process(input_1,input_2)
    begin
        output <= input_1 nand input_2;
    end p1
end arch1;

```

四位二进制加减器:

```

library ieee;
use ieee.std_logic_1164.all;

entity binary_adder is
    port(
        num1,num2 : in std_logic_vector(3 downto 0);
        isSub : in std_logic;
        ans : out std_logic_vector(4 downto 0)
    );
end binary_adder;

architecture arch1 of binary_adder is
    begin
        process(num1,num2,isSub)
            signal exNum1,exNum2 std_logic_vector(4 downto 0)
            begin
                exNum1 <= '0'&num1;

```

```

exNum2 <= '0'&num2;
if (issub = '1') then
    ans <= exNum1 - exNum2;
else
    ans <= exNum1 + exNum2;
end process
end arch1;

```

乘法器：乘法运算法则

```

library ieee;                                --调用库

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

entity cfq is                                --定义实体

    port( a,b:in std_logic_vector(2 downto 0);    --定义输入3位二进制数
        •    y:out std_logic_vector(5 downto 0));    --定义输出6位二进制数

end cfq;                                    --结束实体

architecture a of cfq is                    --定义结构体，描述功能

    •    signal temp1 :std_logic_vector (2 downto 0);    --定义信号1，3位二进制数
    •    signal temp2 :std_logic_vector (3 downto 0);    --定义信号2，4位二进制数
    •    signal temp3 :std_logic_vector (4 downto 0);    --定义信号3，5位二进制数

begin                                        --开始结构体

temp1<=a when b(0) = '1' else "000";    --当(0)位为1时，temp1赋值a，否则为000

temp2<=(a & '0') when b(1)='1' else "0000";--当b(1)位为1时，temp2赋值(a并置0)，否则为0000

temp3<=(a & "00") when b(2)='1' else "00000";--当b(2)位为1时，temp3赋值(a并置00)，否则为00000

    •    y<=temp1+temp2+('0'&temp3);    --y赋值(temp1+temp2+(temp3并置0))

end a;

```


(2) 直接相乘法:

```
library ieee;                                --调用库

use ieee.std_logic_1164.all;

use ieee.std_logic_unsigned.all;

entity cfq is                                --定义实体

    port( a,b:in std_logic_vector(2 downto 0);    --定义输入3位二进制数
    •      y:out std_logic_vector(5 downto 0));    --定义输出6位二进制数

end cfq;                                    --结束实体

architecture a of cfq is                    --定义结构体，描述功能

begin                                        --开始结构体

    y<=a*b;                                --y=a*b

end a;
```

数码管动态扫描:

(1) 单个计数器实现

```
-- Code your design here
library IEEE;
use IEEE.std_logic_1164.all;

entity counter is
    port(
        clc,clk,en : in std_logic;
        output: out std_logic_vector
    );
end counter;

architecture arch1 is
    p1: process(clc,clk,en)
    begin
        if(en = '1')
            if(clc = '1')
                output <= "000";
            end if;
            if(clk ' event and clk = '1')
                output <= output + '1';
            end if;
        end if;
    end process;
end arch1;
```

```



end p1;
end arch1;

```

(3) 计数和数码管同时

3. 七段数码显示原理

<i>a</i>	<i>b</i>	<i>c</i>	<i>d</i>	<i>e</i>	<i>f</i>	<i>g</i>
1	1	1	1	1	1	0
0	1	1	0	0	0	0
1	1	0	1	1	0	1
⋮						

  

共阴极显示器

```

library ieee;          --调用库

use ieee.std_logic_unsigned.all;

use ieee.std_logic_1164.all;

use ieee.std_logic_arith.all;

entity Smg is          --定义实体

port( clk, clr , en: in std_logic;          --定义输入，描述计数器的变量

    •   d0,d1,d2,d3,d4,d5,d6,d7: in std_logic_vector(3 downto 0); --定义输入，描述各个
        数码管显示的变量

    •   seg : out std_logic_vector( 6 downto 0);          --定义输出，段选

    •   scan: out std_logic_vector( 7 downto 0));          --定义输出，位选

end entity Smg;        --结束实体

architecture one of Smg is          --定义结构体，描述功能

    signal count_3: std_logic_vector( 2 downto 0 );          --定义一信号变量，描述计数器值

    signal data: std_logic_vector( 3 downto 0 );              --定义一信号变量，描述瞬时显示值

begin

```

```

process (clk, clr) is      --第一个进程，描述计数器，敏感信号clk、clr

begin

if( clr='1' ) then      --如果clk为1，信号值归零

    •      count_3<="000";

    elsif( clk 'event and clk = '1') then      --如果遇到时钟信号的上升沿

    •      if ( en = '1' ) then      --且使能端为1

    •          if( count_3 = "111" ) then      --如果信号值为“111”归零

    •              count_3<="000";

    •          else

    •              count_3<=count_3+'1';      --否则加一

    •          end if;      --结束if

    end if;      --结束if

end if;      --结束if

end process;      --结束此进程


process ( count_3,d0,d1,d2,d3,d4,d5,d6,d7)      --第二个进程，描述段选，敏感信号为计数值
与d0~d7

begin

    case count_3 is      --选择计数值

    •      when "000" => scan <= "11111110"; data <= d0; --当计数值为0，段选赋值，瞬时显示
值赋值

    •      when "001" => scan <= "11111101"; data <= d1;

    •      when "010" => scan <= "11111011"; data <= d2;

    •      when "011" => scan <= "11110111"; data <= d3;

    •      when "100" => scan <= "11101111"; data <= d4;

    •      when "101" => scan <= "11011111"; data <= d5;

    •      when "110" => scan <= "10111111"; data <= d6;

    •      when "111" => scan <= "01111111"; data <= d7;

    •      when others => scan <= "11111111"; data <= d0; --当其他状况，段选全为一，不使能

```

```

end case;    --结束选择

end process; --结束此进程


process (data)    --第三个进程，位选赋值，敏感信号为瞬时显示值
begin

    case data is    --选择瞬时显示值

        •   when "0000" => seg <= "0111111";    --当瞬时显示值为“0000”，位选为“0111111”，显示0

        •   when "0001" => seg <= "0000110";    --显示1

        •   when "0010" => seg <= "1011011";    --显示2

        •   when "0011" => seg <= "1001111";    --显示3

        •   when "0100" => seg <= "1100110";    --显示4

        •   when "0101" => seg <= "1101101";    --显示5

        •   when "0110" => seg <= "1111101";    --显示6

        •   when "0111" => seg <= "0000111";    --显示7

        •   when "1000" => seg <= "1111111";    --显示8

        •   when "1001" => seg <= "1100111";    --显示9

        •   when "1010" => seg <= "1110111";    --显示a

        •   when "1011" => seg <= "1111100";    --显示b

        •   when "1100" => seg <= "0111001";    --显示c

        •   when "1101" => seg <= "1011110";    --显示d

        •   when "1110" => seg <= "1111001";    --显示e

        •   when "1111" => seg <= "1110001";    --显示f

        •   when others => seg <= "0000000";    --其他情况，位选为0，熄灭

    end case;    --结束选择

    end process;    --结束此进程

end architecture one;    --结束结构体

```

分频器

8分频:

```
-- Code your design here
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;

entity divider_8 is
    port(
        clk_in : in std_logic;
        clk_out: out std_logic;
    );
end divider_8

architecture arch1 of divider is
    signal cnt : std_logic_vector (2 downto 0);
    begin process(clk_in)
        if(cnt /= 3) then
            cnt <= cnt+1;
        else
            cnt <= 0;
            clk_out <= not clk_out;
        end if;
    end process;
end arch1;
```

10分频:

```
library ieee;           --调用库

use ieee.std_logic_1164.all;

use ieee.std_logic_arith.all;

use ieee.std_logic_unsigned.all;

entity SFP is           --定义实体

    port( clk :in std_logic;      --定义输入

        •   fout :out std_logic);  --定义输出

    end SFP;             --结束实体

    architecture one of SFP is    --定义结构体描述功能

        signal countq:std_logic_vector ( 3 downto 0); --定义一四位二进制信号

    begin                --开始结构体
```

```

    process(clk)          --进程，敏感信号为输入

begin

    if clk'event and clk = '1' then    --如果输入发生在上升沿

        if countq/=9 then            --如果信号值不为9

            countq<=countq+1; --信号加一

        else

            countq<=(others => '0' );    --否则信号归零

        end if;    --结束if

    end if;    --结束if

end process;    --结束此进程

process(countq)    --进程，敏感信号为信号变量

begin    --开始进程

    if countq<=1 then    --如果信号小于1

        fout<='1';    --输出为高，即信号为0、1时输出为高

    else

        fout<='0';    --否则输出为低，即信号为2、3、4、5、6、7、8、9时为低

    end if;    --结束if

end process;    --结束进程

end one;    --结束结构体

```

9分频:

奇数分频 一个上升沿触发 一个下降沿触发 两个时钟信号OR即可

```

library ieee;    --调用库

use ieee.std_logic_1164.all;

use ieee.std_logic_arith.all;

use ieee.std_logic_unsigned.all;

entity JFP is    --定义实体

```

```

port( clk :in std_logic;      --定义输入

•   fout :out std_logic); --定义输出

end JFP;      --结束实体

architecture one of JFP is      --定义结构体描述功能

    signal cnt1,cnt2 :integer range 0 to 8;  --定义两信号范围为0~8，即9个数，用于计数

    signal clk1,clk2:std_logic;  --定义两时钟信号，用于或运算

begin      --开始结构体

    process(clk)      --第一个进程，敏感信号为输入

begin

    if clk'event and clk = '1' then  --如果输入发生在上升沿

•   if cnt1 <8 then      --如果计数信号cnt1小于8

•       cnt1<=cnt1+1;  --cnt1加一

•   else

•       cnt1<= 0;      --否则归零

•   end if;

•   if cnt1 <4 then      --如果计数信号小于4

•       clk1<='1';      --时钟信号1为高，即计数信号为0、1、2、3时为高

•   else

•       clk1<='0';      --否则为低，即技术信号为4、5、6、7、8时为低

•   end if;      --结束if

end if;      --结束if

end process;      --结束第一个进程

    process(clk)      --第二个进程，敏感信号为输入

begin

    if clk'event and clk = '0' then  --如果输入发生在下降沿

•   if cnt2 <8 then      --如果计数信号cnt2小于8

```

```

•      cnt2<=cnt2+1;    --cnt2加一

•      else

•      cnt2<= 0;        --否则归零

•      end if;

•      if cnt2 <4 then    --如果计数信号小于4

•      clk2<='1';        --时钟信号2为高，即计数信号为0、1、2、3时为高

•      else

•      clk2<='0';        --否则为低，即技术信号为4、5、6、7、8时为低

•      end if;          --结束if

end if;                --结束if

end process;          --结束第二个进程


      fout <= clk1 or clk2;    --两个时钟信号相或，其中一个时钟信号相对于另一个时钟信号多出
                                半个周期，相或高电平多半个周期实现50%分频

end one;              --结束结构体

```

9分频（输出信号占空比为1/3）

```

library ieee;          --调用库

use ieee.std_logic_1164.all;

use ieee.std_logic_arith.all;

use ieee.std_logic_unsigned.all;

entity JFP is          --定义实体

port( clk :in std_logic;    --定义输入

      fout :out std_logic);  --定义输出

end JFP;              --结束实体

architecture one of JFP is --定义结构体描述功能

    signal countq:std_logic_vector ( 3 downto 0); --定义一四位二进制信号

```



```

begin          --开始结构体

    process(clk)      --进程，敏感信号为输入

begin

    if clk'event and clk = '1' then    --如果输入发生在上升沿

        •   if countq/=8 then          --如果信号值不为9

        •       countq<=countq+1; --信号加一

        •   else

        •       countq<=(others => '0' );    --否则信号归零

        •   end if;    --结束if

        end if;        --结束if

        end process;    --结束此进程

        process(countq)    --进程，敏感信号为信号变量

begin          --开始进程

        if countq<=2 then    --如果信号小于2

        •   fout<='1';    --输出为高，即信号为0、1、3时输出为高

        else

        •   fout<='0';    --否则输出为低，即信号为3、4、5、6、7、8时为低

        end if;        --结束if

        end process;    --结束进程

end one;        --结束结构体

```